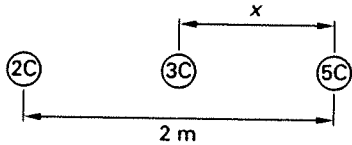


Electrical (9% of morning session questions,  $\frac{11}{120}$ )  
FE - type questions

$\frac{4 \text{ hrs}}{120 \text{ questions}} = 2 \text{ min each. (ave)}$

1. The net force on the center charge is zero for the system of three colinear charges shown. What is the distance  $x$ ?



- (A) 0.77 m
- (B) 1.11 m
- (C) 1.17 m
- (D) 1.23 m

#4226 196

\*6.33 The electric flux passing out through a closed surface is equal to

- a) the line integral of the current around the surface.
- b) zero.
- c) the flux density at the surface.
- d) the total charge enclosed by the surface.

6.36 A point charge of  $2 \times 10^{-7} \text{ C}$  is located at the origin of coordinates. A spherical shell with center at the origin and radius of 20 cm has a surface charge density  $1 \times 10^{-7} \text{ C/m}^2$ . The electric flux density at  $r = 50 \text{ cm}$ , in  $\text{C/m}^2$ , is

- a)  $3.18 \times 10^{-8}$
- b)  $7.96 \times 10^{-8}$
- c)  $9.55 \times 10^{-8}$
- d)  $11.14 \times 10^{-8}$

5. A current of 10 A flows through a 1 mm diameter wire. What is the average number of electrons that pass through a cross section of the wire per second?

- (A)  $1.6 \times 10^{18} \text{ e/s}$
- (B)  $6.2 \times 10^{18} \text{ e/s}$
- (C)  $1.6 \times 10^{19} \text{ e/s}$
- (D)  $6.3 \times 10^{19} \text{ e/s}$


\*6.34 The direction of the force acting on a moving charge placed in a magnetic field is

- a) perpendicular to the magnetic field.
- b) opposite to the direction of motion of the charge.
- c) along the direction of the magnetic field.
- d) along the direction of motion of the charge.

\*6.41 Two long, straight conductors located at  $(0,3,z)$  and  $(0,-3,z)$  each carry 5 amperes in the same direction (distances are in meters). The magnitude of magnetic field intensity at  $(4,0,0)$  is

- a)  $1/\pi$
- b)  $2/5\pi$
- c)  $3/5\pi$
- d)  $4/5\pi$

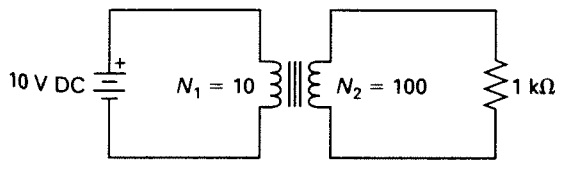14. How much power is dissipated by the 1 kΩ resistor?




- (A) 0 W
- (B) 0.1 W
- (C) 1 W
- (D) 10 W

2. A heating element consists of two wires of different materials connected in series. At 20°C, they have resistances of 600 Ω and 300 Ω, and average temperature coefficients of 0.001 1/°C and 0.004 1/°C, respectively. What is the heating element's total resistance at 50°C?

- (A) 900 Ω
- (B) 950 Ω
- (C) 980 Ω
- (D) 990 Ω


\*6.1 For the circuit below, with voltages' polarities as shown, KVL in equation form is

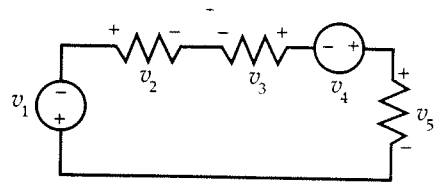- a)  $v_1 + v_2 + v_3 - v_4 + v_5 = 0$
- b)  $-v_1 + v_2 + v_3 - v_4 + v_5 = 0$
- c)  $v_1 + v_2 - v_3 - v_4 + v_5 = 0$
- d)  $-v_1 - v_2 - v_3 + v_4 + v_5 = 0$




\*6.4 For the circuit shown, the voltage across the 4 ohm resistor is, with  $v = 1\text{ V}$

- a) 1/4
- b) 1/2
- c) 2/3
- d) 2

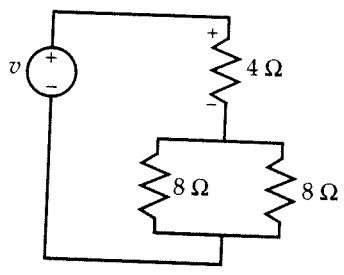

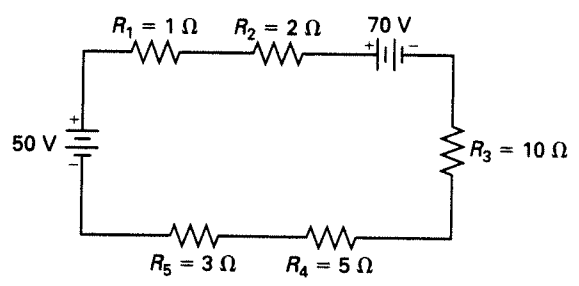
6. What is the voltage across the 10 Ω resistor in the circuit shown?



- (A) 9.5 V
- (B) 24 V
- (C) 33 V
- (D) 57 V


\*6.3 Find the magnitude and sign of the power, in watts, absorbed by the circuit element in the box.

- a) -20
- b) -8
- c) 8
- d) 12

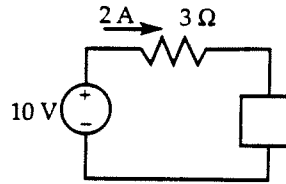


6.7 The power delivered to the 5 ohm resistor is

- a) 1.5
- b) 2.15
- c) 2.85
- d) 3.2

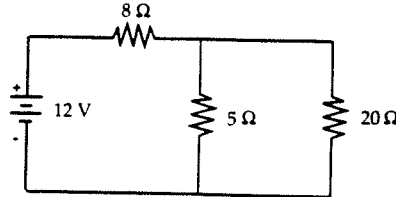

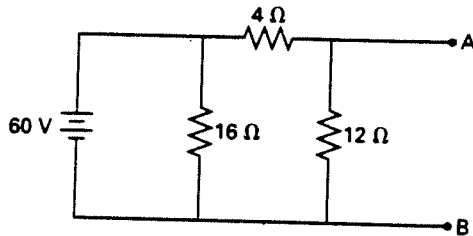
7. What are the Thevenin equivalent resistance and voltage between terminals A and B?



- (A)  $R_{Th} = 3 \Omega, V_{Th} = 45 \text{ V}$
- (B)  $R_{Th} = 7.5 \Omega, V_{Th} = 7.5 \text{ V}$
- (C)  $R_{Th} = 7.5 \Omega, V_{Th} = 60 \text{ V}$
- (D)  $R_{Th} = 12 \Omega, V_{Th} = 5 \text{ V}$

6.29 A  $100 \mu\text{F}$  capacitor has  $I_C(t)$ . The capacitor voltage  $V_C(t)$  at  $t = 2.5$  seconds ( $V(0) = 1.0 \text{ V}$ ) is most nearly


- a) -24
- b) -25
- c) 25
- d) 26

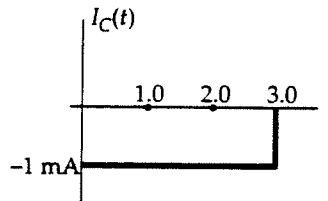

6.30 The voltage across a  $10 \mu\text{F}$  capacitor is  $50t^2 \text{ V}$ . The time, in seconds, it will take to store 200 J of energy is most nearly

- a) 0.15
- b) 0.21
- c) 1.38
- d) 11.25

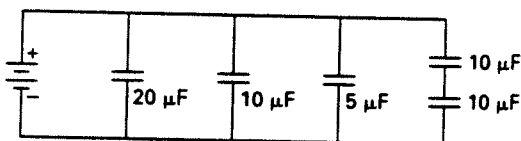22. What is the equivalent capacitance seen by the battery for the circuit shown?




- (A)  $3 \mu\text{F}$
- (B)  $30 \mu\text{F}$
- (C)  $40 \mu\text{F}$
- (D)  $50 \mu\text{F}$

15. A 10-microfarad capacitor has been charged to a potential of 150 volts. A resistor of  $25\ \Omega$  is then connected across the capacitor through a switch. When the switch is closed for 10 time constants, the total energy dissipated by the resistor is most nearly

- (A)  $1.0 \times 10^{-7}$  joules
- (B)  $1.1 \times 10^{-1}$  joules
- (C)  $9.0 \times 10^1$  joules
- (D)  $9.0 \times 10^3$  joules

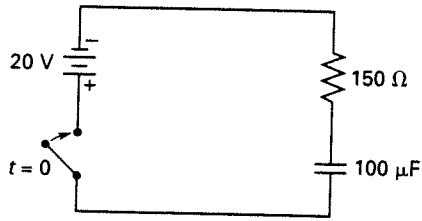
28. The switch in the circuit shown is closed at  $t = 0$ . How long will it take to charge the capacitor to 80% of the battery voltage?



- (A) 2.0 ms
- (B) 10 ms
- (C) 12 ms
- (D) 24 ms


#1644 689

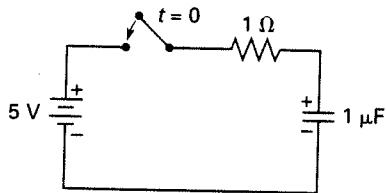29. The initial voltage across the capacitor is 2.5 V. The switch is closed at  $t = 0$ . What is the current at  $t = 0$  s?




- (A) 0.2 A
- (B) 0.7 A
- (C) 1.0 A
- (D) 2.5 A

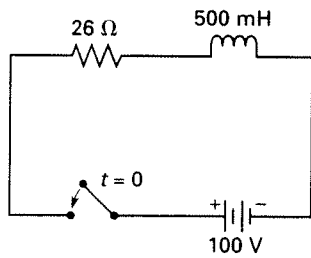27. The switch in the circuit shown is closed at  $t = 0$ .  
What is the voltage across the inductor at  $t = 30 \text{ ms}$ ?



- (A) 1.0 V  
(B) 19 V  
(C) 21 V  
(D) 48 V

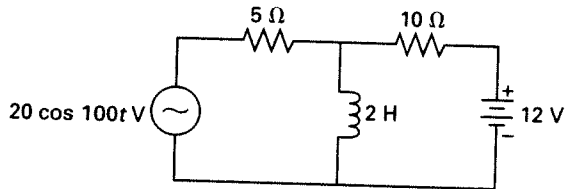
31. What is the average DC current through the inductor?




- (A) 0 A  
(B) 0.8 A  
(C) 1.2 A  
(D) 3.2 A

- 6.51 Given the voltages into the following OP-AMP network, the output voltage is

- a) -2  
b) -4  
c) -7  
d) -10

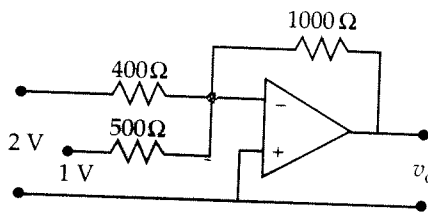

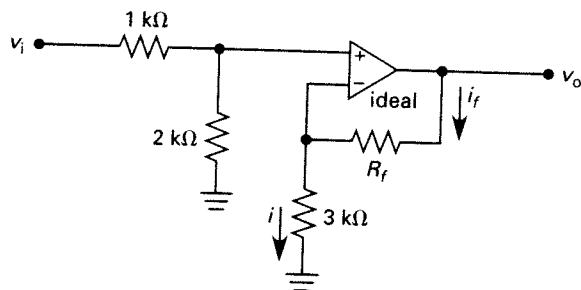4. For the ideal op amp shown, what should be the value of resistor  $R_f$  to obtain a gain of 5?




- (A) 12.0 kΩ  
(B) 19.5 kΩ  
(C) 22.5 kΩ  
(D) 27.0 kΩ

\*6.12  $(2 + j2)(3 - j4)$  is most nearly


- a)  $6.0 \angle -21.8^\circ$    b)  $14.1 \angle -21.8^\circ$    c)  $14.1 \angle -8.1^\circ$    d)  $28.0 \angle -8.1^\circ$

\*6.13 The following sinusoid is displayed on an oscilloscope. The RMS voltage and the radian frequency are most nearly

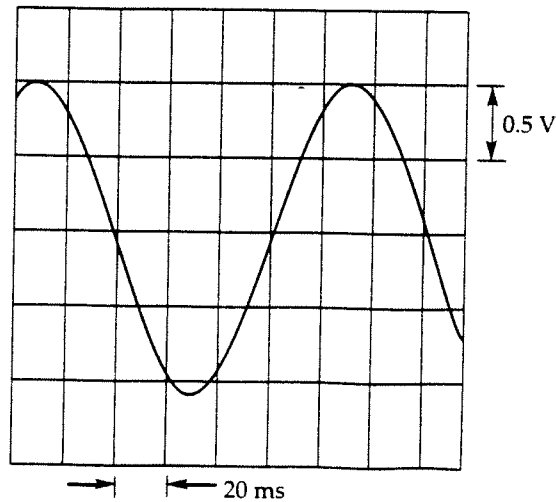- a) 1, 8.33  
 b) 0.7071, 52.36  
 c) 1.4142, 52.36  
 d) 2, 8.33



26.

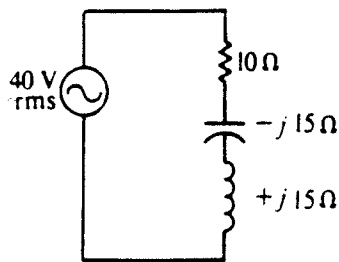


What is the magnitude of the steady-state, root-mean-square voltage across the capacitor in the circuit shown above?

- (A) 15 V  
 (B) 30 V  
 (C) 45 V  
 (D) 60 V  
 (E) 75 V

6.18 The current through the capacitor is

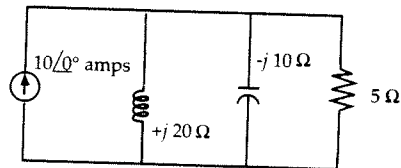
- a) 0.21 A  
 b) 0.57 A  
 c) 1.0 A  
 d) 4.85 A




6.19 The voltage across the 5-ohm resistor of Problem 6.18 is

- a) 0.50 V  
 b) 1.61 V  
 c) 2.06 V  
 d) 48.5 V

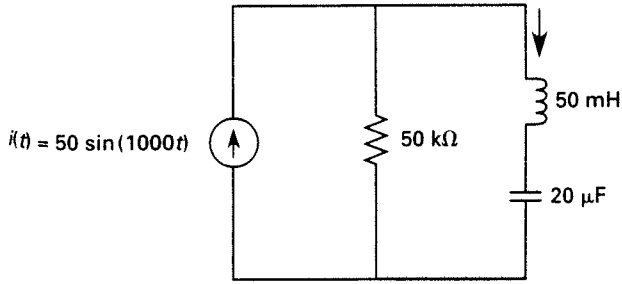2. What is the current through the  $LC$  leg of the following circuit?



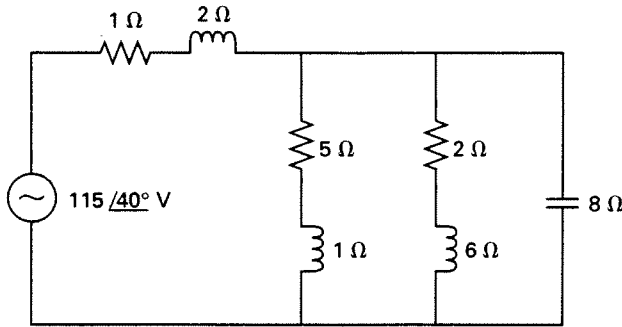- (A) 0
- (B)  $50 \sin(1000t)$  A
- (C)  $50 \sin\left(1000t + \frac{\pi}{4}\right)$  A
- (D)  $70.7 \sin\left(1000t - \frac{3\pi}{4}\right)$  A




3. What is the average power dissipated by the circuit?

- (A) 24 W
- (B) 765 W
- (C) 910 W
- (D) 1970 W

6. A 13.2 kV circuit has a 10 000 kVA load with a 0.85 lagging power factor. How much capacitive reactive power (in kVAR) is needed to correct the power factor to 0.97 lagging?

- (A) 2500 kVAR
- (B) 3138 kVAR
- (C) 4753 kVAR
- (D) 5156 kVAR

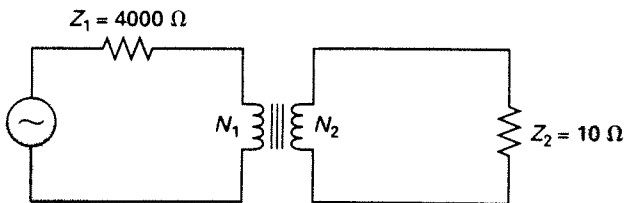7. What is the turns ratio ( $N_1 : N_2$ ) for maximum power transfer in the following circuit?



- (A) 1:40
- (B) 1:20
- (C) 20:1
- (D) 40:1

Answers

1 D	6.33 d	6.36 b	5 D	6.34 a	6.41 d	14 A	2 B	6.1 c	6.4 b	6 A
6.3 c	6.7 d	7 A	6.29 a	6.30 d	22 c	15 B	28 D	29 D	27 C	31 C
6.51 c	4 B	6.12 c	6.13 b	26 D	6.18 d	6.19 d	2 B	3 A	6 B	7 C